COKOINO Timer Alarm Clock & Watering System Kit

Table

1. Preface 2

2. Product List 2

3. Kit Courses and Corresponding Code 5

4. Safety and Notes 6

5. What's more 6

Support : Cokoino@outlook.com

1. Preface

Thank you for purchasing and using this Timing Alarm Clock & Watering System Kit from COKOINO.

COKOINO has been committed to the development of STEM projects, providing engaging products and comprehensive tutorials. It guides programming enthusiasts and students to complete projects by hand, helping them understand the application scenarios of knowledge through practice.

The Timing Alarm Clock & Watering System Kit is an all-in-one Arduino-based kit. It not only boasts the features of an educational kit, with abundant courses and code resources included, allowing users to grasp the theoretical knowledge of various electronic modules during hands-on practice, enhance their practical operation skills, strengthen their logical thinking abilities and improve their programming proficiency; but also has practical real-world applications. Users can use it as an ordinary alarm clock, or follow the tutorials to build a watering system to water their favorite plants on a regular schedule. The kit comes with a 5-meter black hose, 3 sprinkler drippers, and a high-flow water pump, supporting watering up to 3 plants at the same time. Equipped with a power adapter, there is no need to worry about long-term power supply. The kit is stable, reliable and has a long service life.

2. Product List

UNO R3 Board 1PCS	Expansion Board for UNO 1PCS	5V Relay Module 1PCS
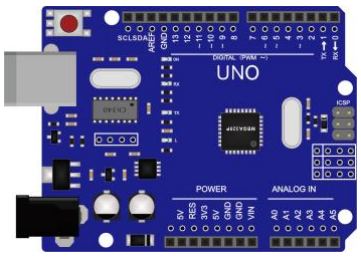	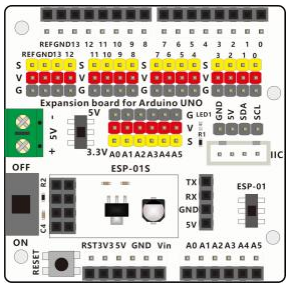	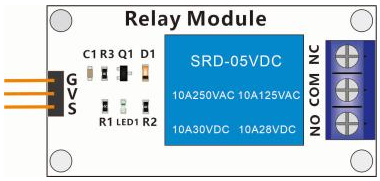
Passive Buzzer Module 1PCS	**Red LED Module 1PCS**	**Green LED Module 1PCS**

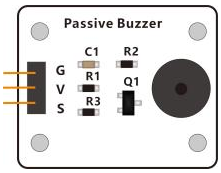	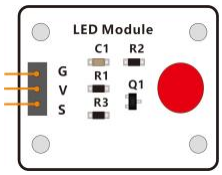	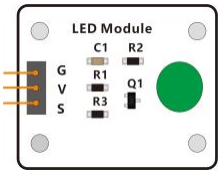
Red Button Module 1PCS	**Green Button Module 1PCS**	**Yellow Button Module 1PCS**
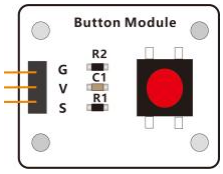	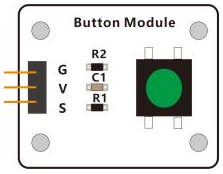	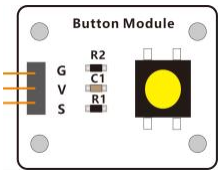
Blue Button Module 1PCS	**Power Adapter Board 1PCS**	**1602 LCD Module 1PCS**
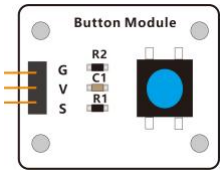	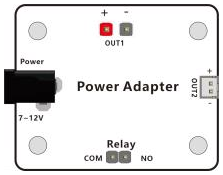	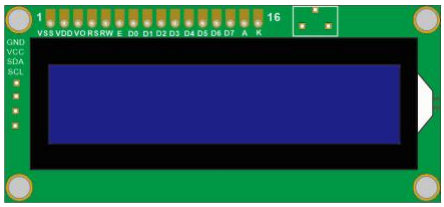
Water Pump 1 PCS	**DS1302 RTC Module 1PCS**	**9V 1A Adapter**
	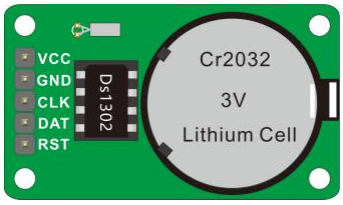	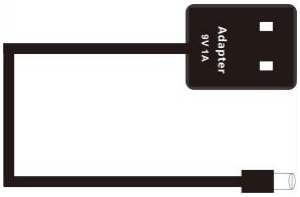
(Black,Red,Yellow)150mm Female-to-Female 3-Pin Integrated Dupont Cable 8PCS	**(Black, Red) 150mm Female-to-Female 2-Pin Integrated Dupont Cable 1PCS**	**(Black, Red) 100mm Male-to-Female 2-Pin (Individual) Dupont Cable 1PCS**

Support : Cokoino@outlook.com

(Red, Black, Yellow, Green, Blue) 150mm Female-to-Female 5-Pin (One End Integrated + One End Individual) Dupont Cable 1PCS	(Yellow, Green) 150mm Male-to-Female 2-Pin (Individual) Dupont Cable 1PCS	170mm 1602LCD Connection Cable, 4-Pin (XH2.54) 1PCS
4/7 black soft rubber hose(5m)	Drip irrigation nozzle 3PCS	Tee fitting 3PCS
Plug 2PCS	M3×14mm Countersunk head screw 6PCS	M3×3mm Nylon nut 4PCS
M3×8mm Round Head Screw 32PCS	M3 Nut 30PCS	M3*6mm+6mm copper column 25PCS
M3*60mm copper column	A to B USB cable 1PCS	

Support : Cokoino@outlook.com

4PCS		

3. Kit Courses and Corresponding Code

The tutorial of this kit includes abundant courses and Arduino code.

Lesson 1 introduces Arduino IDE and its installation method.

Lesson 2 introduces our expansion board based on Arduino UNO.

Lessons 3 to 9 cover the theoretical knowledge and sample applications of all modules of this kit, with highly detailed hardware connection diagrams provided for each lesson. Users can refer to the diagrams to build test environments and complete sample experiments; alternatively, they can combine the existing modules to develop more complex and interesting experiments.

Lesson 10 elaborates on the assembly steps of the Timer Alarm & Watering Device.

Lesson 11 introduces how to use the alarm clock function of the Timer Alarm & Watering Device.

Lesson 12 demonstrates how to build a watering system based on the Timer Alarm & Watering Device. You can also upload different sets of code to the Arduino UNO, enabling the system to perform various watering functions—such as cyclic countdown watering, daily scheduled watering, and weekly scheduled watering.

We recommend learning and using this kit **step by step** in the order of the lessons. If you are an experienced user, you may skip Lessons 1 to 9 entirely, start directly with **Lesson 10** to assemble the Timer Alarm & Watering Device, and then proceed to the experiments in either **Lesson 11** or **Lesson 12**.

4. Safety and Notes

4.1 Please refer to the document CKK0021-main\ Tutorial\Lesson 10 How to Assemble the Cokoino Timer Alarm & Watering device. Pay attention to the specifications of the screws to prevent using them in the wrong place.

4.2 Before powering on, please make sure that all connected circuits are not short-circuited, especially 5V and GND.A short circuit can cause high current in your circuit, create excessive component heat and cause permanent damage to your hardware!

4.3 It is not protected against rain or snow, so it is recommended for **indoor use only**.

5. What's more

Let's start your experiment. Wish you a great time and fruitful gains.